

## Half Adder

The half adder adds two single binary digits A and B. It has two outputs, sum (S) and carry (C). The carry signal represents an overflow into the next digit of a multi-digit addition.

The simplest half-adder design incorporates an XOR gate for S and an AND gate for C.

