D Flip Flop

The output of the D Flip Flop is same as that of its input. The D stands for "data"; this flip-flop stores the value that is on the data line. It can be thought of as a basic memory cell.